

LAB REPORT

Audio Amplifier (STEREO)

Aim → To construct a stereo audio amplifier circuit and demonstrate its functioning.

Components used →

- 1) LM386 Low Voltage Audio Power Amplifier IC (x2)
- 2) 7-10 W Speaker (x2)
- 3) Audio Jack
- 4) 4-12 V DC Input
- 5) 10 μ F capacitor (x6)
- 6) 4.7 μ F capacitor (x2)
- 7) 220 μ F, 16V capacitor (x2)
- 8) 100 μ F capacitor (x2)
- 9) 10 Ω resistor (x2)
- 10) 104 pF capacitor (x2)
- 11) 1K Ω Potentiometer

Experimental Setup & functioning

i) LM386 Low Voltage Audio Power Amplifier IC
→ It has the function of a low-voltage audio amplifier with gain from 20 to 200. It has 8 pins, whose functions are listed below:

a) PIN 1, 8 → Gain controlling pins
→ They are used to adjust gain of amplifier.

b) PIN 2, 3 → Input pins

⇒ PIN 2 is the negative input terminal connected to ground.

PIN 3 is the positive input terminal connected to the device.

c) PIN 4, 6 → Power supply pins

⇒ PIN 4 is connected to ground.

PIN 6 is connected to ~~the~~ positive ^{terminal} ~~capacitors~~ of power supply.
(4-12 Volts)

PIN 5

d) Output pin → The amplified sound signal is output from this pin. To remove any high sudden frequencies / noise an RC filter with $R = 10 \Omega$ and $C = 4.7 \mu F$ is used.

e) PIN 7

Bypass terminal → This terminal can be left open or grounded using $10 \mu F$ capacitor for stability.

2) Speaker → Outputs the amplified audio signal which is connected across ~~220~~ μF capacitor and ground.

3) Audio jack → Used for taking input from phone or laptop.

4) 1K Variable resistor

→ Adjusts the magnitude of input signal.

Results

1) For $f = 528 \text{ Hz}$ (Input signal)

$$V_i = 0.055 \text{ V}$$

$$V_o = 11.14 \text{ V}$$

$$\Rightarrow \text{Gain} = \frac{V_o}{V_i} = \frac{11.14}{0.055} \approx 202.54$$


Conclusion

→ The circuit successfully amplified the input audio signal. The experimental gain values were close to the expected gain values.

Precautions

- Ensure that polarity of electrolytic capacitors is taken care of while connecting them.
- Keep the input voltage between 4-12 volts as this is the operational range of LM386 IC.

Circuit Diagram

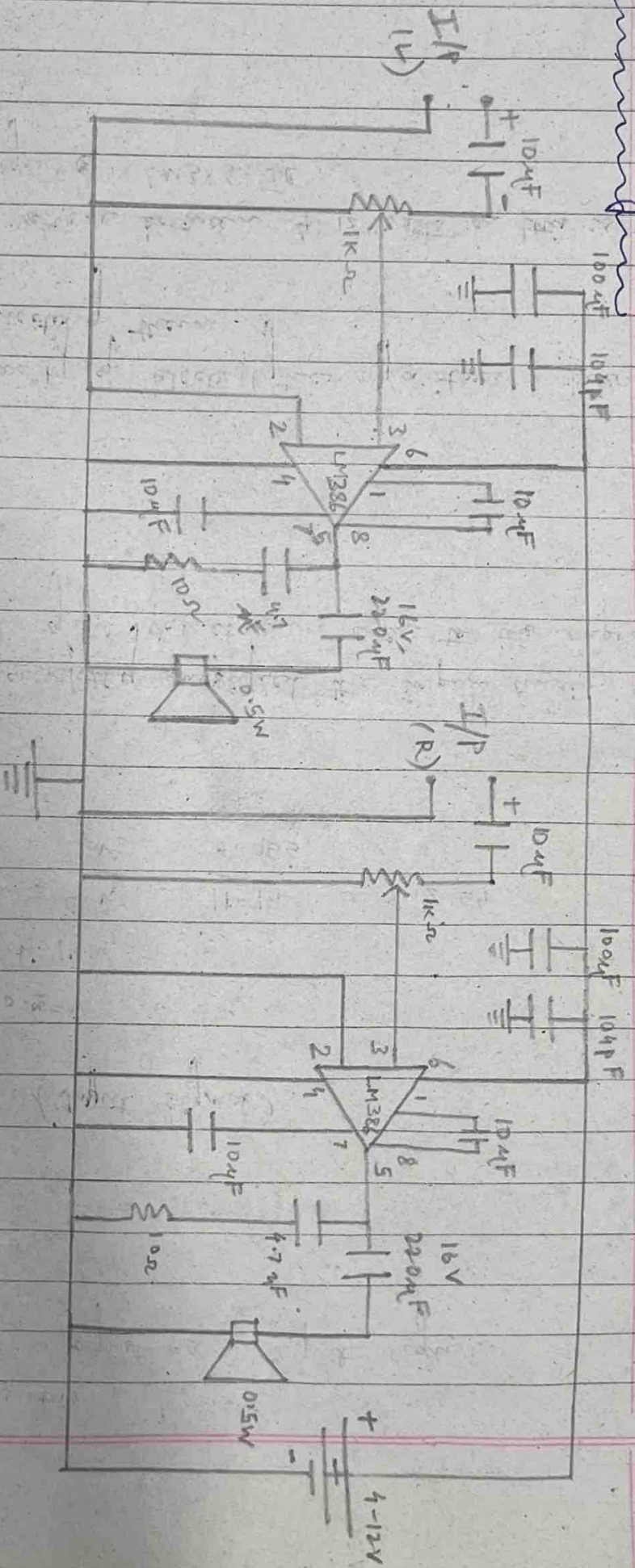

Audio Amplifier (Stereo)