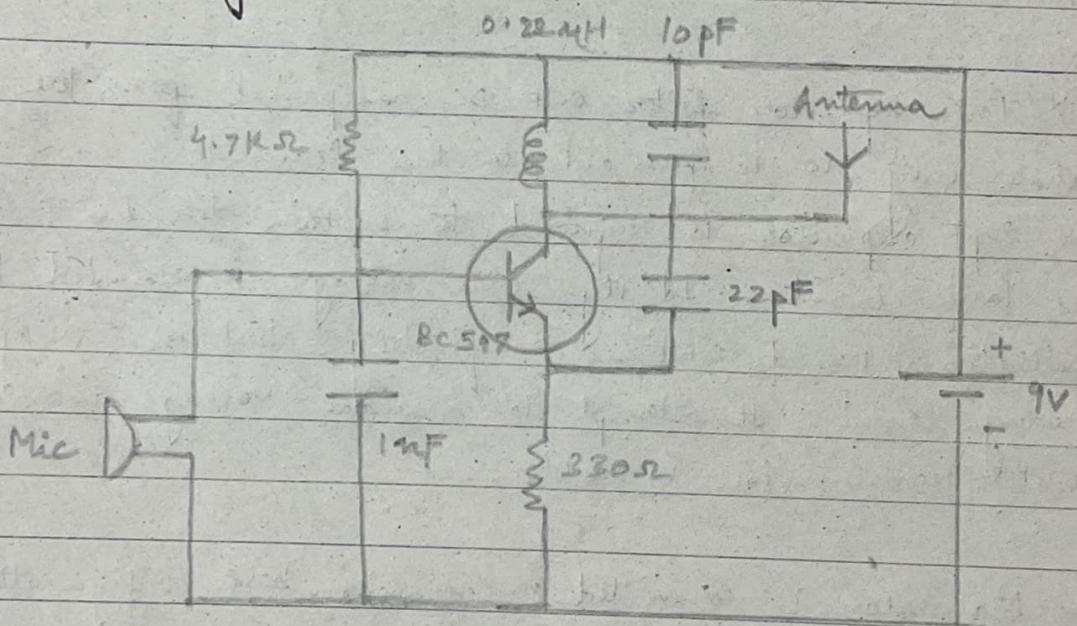


# FM TRANSMITTER

Aim → To design and build a FM transmitter using a single transistor.

Components used →  $320\Omega$ ,  $4.7\text{ k}\Omega$  resistor,  $0.22\mu\text{H}$  inductor,  $2 \times 10\text{pF}$ ,  $22\text{pF}$ ,  $1\text{nF}$  capacitors, 1 microphone, antenna,  $9\text{V}$  power source, BC547 transistor.

Circuit diagram →



Working of circuit →

- (i) OSCILLATOR ⇒ The transistor acts as oscillator and amplifier of the input signal. The  $0.22\mu\text{H}$  inductor and  $10\text{pF}$  capacitor form a tuned LC tank circuit. The values of L and C determine the carrier frequency (frequency at which radio waves are transmitted).

$$f = \frac{1}{2\pi\sqrt{LC}}$$

FM broadcast band lies between 88 MHz - 108 MHz. This is a Colpitts' oscillator (an oscillator that can generate sinusoidal waves of high frequency)

iii) MODULATOR  $\Rightarrow$  Input audio signals from the microphone are coupled to the transistor's base by the  $1\text{nF}$  capacitor. Variations in the input signals modulate the transistor's base current, which in turn causes variations in the carrier signal.

The  $1\text{nF}$  capacitor filters out DC component from the input and allows only AC to pass out to the transistor.

The  $2\text{pF}$  capacitor is required to sustain the  $Lc$  oscillations in the tank circuit. Ideally, once voltage is provided the  $Lc$  oscillations would continue indefinitely, but in reality there are heavy losses. It attempts to maintain voltage across circuit so that transmission is stable.

The transistor is connected in common base configuration.

$$\alpha \text{ (current gain)} = \frac{I_c}{I_E}$$

The  $330\Omega$  resistor maintains  $V_E$  which ensures that there is a gain across the transistor.

$$\Rightarrow \text{Voltage gain} ; A = \frac{\beta R_C}{R_B} , \beta = \frac{\alpha}{(1-\alpha)}$$

(iii) ANTENNA  $\Rightarrow$  The modulated signal from the transistor is amplified and fed ~~into~~ into the antenna which broadcasts the signal at the resonant frequency. Ideally, length of antenna should be high, for better transmission.

Observations  $\rightarrow$  Values of C were changed to get output frequency between 88 MHz - 108 MHz.

$$\text{For } L = 0.22 \mu\text{H}$$

$$C_1 = 20 \mu\text{F} \Rightarrow f = \frac{1}{2\pi\sqrt{L+C_1}} = 75.9 \text{ MHz} \quad (\text{not in range})$$

$$C_2 = 10 \mu\text{F} \Rightarrow f = \frac{1}{2\pi\sqrt{L+C_2}} = 107.3 \text{ MHz} \quad (\text{in range})$$

A longer antenna produced a clearer output.

Results  $\rightarrow$  In conclusion, this experiment demonstrates the practical applications of signal processing and transmission.

Precautions  $\rightarrow$

- Ensure power source is turned off before making any changes in circuit to prevent shocks.
- The 330 $\Omega$  resistor was observed to heat up significantly. So, take readings when components are cool.